

[3] [30 points]


A sequential system is described with the state table shown.

S	Input		Output
	x=0	x=1	
A	A	E	0
B	E	A	0
C	B	F	0
D	F	B	1
E	C	G	0
F	G	C	0
G	D	H	0
H	H	D	1
	S*		

Design a synchronous state machine that implements the sequential system using Enabled T Flip-Flops. Rename the states using a three-bit binary code, so that A becomes 000, B becomes 001, etc.

Bonus [10 points]

 Implement the next-state logic (NSL) of the synchronous state machine using ROMs. Show the ROMs' logic diagrams and the tables of their addresses (inputs) and contents (data outputs).



S	x	Q ₂	Q ₁	Q ₀	S*	Q ₂ *	Q ₁ *	Q ₀ *	EN ₂	EN ₁	EN ₀
A	0	0	0	0	A	0	0	0	0	0	0
B	0	0	0	1	E	0	0	1	0	0	0
C	0	0	1	0	B	0	1	0	0	0	0
D	0	0	1	1	F	0	1	1	0	0	0
E	0	1	0	0	G	1	0	0	0	0	0
F	0	1	0	1	A	1	0	1	0	0	0
G	0	1	1	0	E	1	1	0	0	0	0
H	0	1	1	1	B	1	1	1	0	0	0
A	1	0	0	0	A	0	0	0	1	1	1
B	1	0	0	1	E	0	0	1	1	1	1
C	1	0	1	0	B	0	1	0	1	1	1
D	1	0	1	1	F	0	1	1	1	1	1
E	1	1	0	0	G	1	0	0	1	1	1
F	1	1	0	1	A	1	0	1	1	1	1
G	1	1	1	0	E	1	1	0	1	1	1
H	1	1	1	1	B	1	1	1	1	1	1

$$\begin{aligned}
 EN_0 &= Q_0 \oplus Q_1 \\
 EN_1 &= Q_0 \oplus Q_2 \\
 EN_2 &= x'(Q_0 \oplus Q_2) + x(Q_0 \oplus Q_2) \\
 &= x \oplus Q_0 \oplus Q_2
 \end{aligned}$$